

CPU Design Project Phase 1 Submission

DataPath:

```
module DataPath(
    input wire clock, clear,
    input wire [31:0] Mdatain,
    input wire [4:0] ops,

    input RAout, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out,
    RYout, RZHIout, RZLOout, PCout, IROUT, HIout, LOout, MDRout, PORTout,

    input RAIN, R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in, R14in, R15in,
    RYin, RZin, PCin, IRin, HIin, LOin, MDRin, PORTin, Read
);

wire [31:0] BusMuxOut, BusMuxInRA, BusMuxInR0, BusMuxInR1, BusMuxInR2, BusMuxInR3, BusMuxInR4, BusMuxInR5, BusMuxInR6, BusMuxInR7, BusMuxInR8,
BusMuxInR9, BusMuxInR10, BusMuxInR11, BusMuxInR12, BusMuxInR13, BusMuxInR14, BusMuxInR15, Rydataout, BusMuxInHI, BusMuxInLO, BusMuxInRZHI, BusMuxInRZLO,
BusMuxInPC, BusMuxInMDR, BusMuxInPort;

wire [63:0] Zregin;

register RA(clear, clock, RAIN, RegisterAImmediate, BusMuxInRA);

register R0(clear, clock, R0in, BusMuxOut, BusMuxInR0);
register R1(clear, clock, R1in, BusMuxOut, BusMuxInR1);
register R2(clear, clock, R2in, BusMuxOut, BusMuxInR2);
register R3(clear, clock, R3in, BusMuxOut, BusMuxInR3);
register R4(clear, clock, R4in, BusMuxOut, BusMuxInR4);
register R5(clear, clock, R5in, BusMuxOut, BusMuxInR5);
register R6(clear, clock, R6in, BusMuxOut, BusMuxInR6);
register R7(clear, clock, R7in, BusMuxOut, BusMuxInR7);
register R8(clear, clock, R8in, BusMuxOut, BusMuxInR8);
register R9(clear, clock, R9in, BusMuxOut, BusMuxInR9);
register R10(clear, clock, R10in, BusMuxOut, BusMuxInR10);
register R11(clear, clock, R11in, BusMuxOut, BusMuxInR11);
register R12(clear, clock, R12in, BusMuxOut, BusMuxInR12);
register R13(clear, clock, R13in, BusMuxOut, BusMuxInR13);
register R14(clear, clock, R14in, BusMuxOut, BusMuxInR14);
register R15(clear, clock, R15in, BusMuxOut, BusMuxInR15);
register RY(clear, clock, RYin, BusMuxOut, Rydataout);
register RZHI(clear, clock, RZin, Zregin[63:32], BusMuxInRZHI);
register RZLO(clear, clock, RZin, Zregin[31:0], BusMuxInRZLO);
register PC(clear, clock, PCin, BusMuxOut, BusMuxInPC);
register IR(clear, clock, IRin, BusMuxOut, BusMuxInIR);
register HI(clear, clock, HIin, BusMuxOut, BusMuxInHI);
register LO(clear, clock, LOin, BusMuxOut, BusMuxInLO);

mdrReg MDR(clear, clock, MDRin, Read, Mdatain, BusMuxOut, BusMuxInMDR);

alu alu(ops, Rydataout, BusMuxOut, Zregin);

//ADD add(Rydataout, BusMuxOut, Zregin);

Bus bus(BusMuxInRA, BusMuxInR0, BusMuxInR1, BusMuxInR2, BusMuxInR3, BusMuxInR4, BusMuxInR5, BusMuxInR6, BusMuxInR7, BusMuxInR8,
BusMuxInR9, BusMuxInR10, BusMuxInR11, BusMuxInR12, BusMuxInR13, BusMuxInR14, BusMuxInR15, BusMuxInHI, BusMuxInLO, BusMuxInRZHI, BusMuxInRZLO,
BusMuxInPC, BusMuxInMDR, BusMuxInPort, RAout, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out,
R13out, R14out, R15out, RYout, RZHIout, RZLOout, PCout, IROUT, HIout, LOout, MDRout, PORTout, BusMuxOut);

endmodule
```

Bus:

```
module Bus (
    input [31:0] BusMuxInRA, BusMuxInR0, BusMuxInR1, BusMuxInR2, BusMuxInR3, BusMuxInR4, BusMuxInR5, BusMuxInR6, BusMuxInR7, BusMuxInR8,
    BusMuxInR9, BusMuxInR10, BusMuxInR11, BusMuxInR12, BusMuxInR13, BusMuxInR14, BusMuxInR15, BusMuxInHI, BusMuxInLO, BusMuxInRZHI, BusMuxInRZLO,
    BusMuxInPC, BusMuxInMDR, BusMuxInPort,

    input RAout, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out,
    RYout, RZHIout, RZLOout, PCout, IROUT, HIout, LOout, MDRout, PORTout,

    output wire [31:0] BusMuxOut
);

reg [31:0] q;

always @ (*) begin
    if(RAout) q = BusMuxInRA;

    if(R0out) q = BusMuxInR0;
    if(R1out) q = BusMuxInR1;
    if(R2out) q = BusMuxInR2;
    if(R3out) q = BusMuxInR3;
    if(R4out) q = BusMuxInR4;
    if(R5out) q = BusMuxInR5;
    if(R6out) q = BusMuxInR6;
    if(R7out) q = BusMuxInR7;
    if(R8out) q = BusMuxInR8;
    if(R9out) q = BusMuxInR9;
    if(R10out) q = BusMuxInR10;
    if(R11out) q = BusMuxInR11;
    if(R12out) q = BusMuxInR12;
    if(R13out) q = BusMuxInR13;
    if(R14out) q = BusMuxInR14;
    if(R15out) q = BusMuxInR15;
    if(PCout) q = BusMuxInPC;
    if(HIout) q = BusMuxInHI;
    if(LOout) q = BusMuxInLO;
    if(MDRout) q = BusMuxInMDR;
    if(RZHIout) q = BusMuxInRZHI;
    if(RZLOout) q = BusMuxInRZLO;
    if(PORTout) q = BusMuxInPort;
end
assign BusMuxOut = q;
endmodule
```

Register file:

```
module register(  
    input clear, clock, enable,  
    input [31:0] BusMuxOut,  
    output wire [31:0] BusMuxIn  
);  
reg [31:0] q;  
initial q = 32'b0;  
always @ (posedge clock)  
begin  
    if (clear) begin  
        q <= {32{1'b0}};  
    end  
    else if (enable) begin  
        q <= BusMuxOut;  
    end  
end  
assign BusMuxIn = q[31:0];  
endmodule  
|
```

MDR Register file:

```
module mdrReg(  
    input clear, clock, MDRin, Read,  
    input [31:0] Mdatain, BusMuxOut,  
    output [31:0] BusMuxIn  
);  
reg [31:0] mdrregdata;  
initial mdrregdata = 8'h0;  
always @ (posedge clock)  
begin  
    if (clear) begin  
        mdrregdata <= {32{1'b0}};  
    end  
    else if (MDRin) begin  
        case (Read)  
            // mdrregdata = 32'h10101010;  
            1'b0 : mdrregdata = BusMuxOut;  
            1'b1 : mdrregdata = Mdatain;  
        endcase  
    end  
end  
assign BusMuxIn = mdrregdata;  
endmodule  
|
```

ALU:

```

module alu(
    input [4:0] ops,
    input [31:0] A, B,
    output reg [63:0] Zregin
);

//reg [63:0] x;

wire [31:0] addresult, andresult, orresult, notresult, negresult, rorresult, rolresult, shlresult, shrresult, shraresult, subresult;
wire [63:0] mulresult, divresult;

ADD ADD(A, B, addresult);
AND_mod AND_mod(A, B, andresult);
OR_mod OR_mod(A, B, orresult);
NOT_mod NOT_mod(A, notresult);
NEG NEG(A, negresult);
MUL MUL(A, B, mulresult);
ROR ROR(A, B, rorresult);
ROL ROL(A, B, rolresult);
SHL SHL(A, B, shlresult);
SHR SHR(A, B, shrresult);
SHRA SHRA(A, B, shraresult);
SUB SUB(A, B, subresult);
DIV DIV(A, B, divresult);

//... continue this

//NEED TO IMPLEMENT AND, OR, SUB, MUL, DIV, SHR, SHRA, SHL, ROR, ROL, NEG, NOT

//addresult or andresult or orresult or notresult or negresult or rorresult or rolresult or shlresult or shrresult or shraresult or mulresult

always @(*) begin
    case(ops)
        5'b00000: Zregin = addresult;
        5'b00001: Zregin = andresult;
        5'b00010: Zregin = orresult;
        5'b00011: Zregin = notresult;
        5'b00100: Zregin = negresult;
        5'b00101: Zregin = mulresult;
        5'b00110: Zregin = rorresult;
        5'b00111: Zregin = rolresult;
        5'b01000: Zregin = shlresult;
        5'b01001: Zregin = shrresult;
        5'b01010: Zregin = shraresult;
        5'b01011: Zregin = divresult;
        5'b01100: Zregin = subresult;
        // 5'b01101: x = bmi_13;
        // 5'b01110: q = bmi_14;
        // 5'b01111: q = bmi_15;
        // 5'b10000: q = bmi_16;
        // 5'b10001: q = bmi_17;
        // 5'b10010: q = bmi_18;
        // 5'b10011: q = bmi_19;
        // 5'b10100: q = bmi_20;
        // 5'b10101: q = bmi_21;
        // 5'b10110: q = bmi_22;
        // 5'b10111: q = bmi_23;
        // 5'b11000: q = bmi_24;
        // 5'b11001: q = bmi_25;
        // 5'b11010: q = bmi_26;
        // 5'b11011: q = bmi_27;
        // 5'b11100: q = bmi_28;
        // 5'b11101: q = bmi_29;
        // 5'b11110: q = bmi_30;
        // 5'b11111: q = bmi_31;
    endcase
end

//assign Zregin = x;

endmodule

```

ADD module:

```
// Ripple Carry ADD module
module ADD(A, B, addressult);

input [31:0] A, B;
output [31:0] addressult;

reg [31:0] addressult;
reg [32:0] LocalCarry;

integer i;

always@(A or B)
begin
    LocalCarry = 32'b0;
    for(i = 0; i < 32; i = i + 1)
    begin
        addressult[i] = A[i]^B[i]^ LocalCarry[i];
        LocalCarry[i+1] = (A[i]&B[i])|(LocalCarry[i]&(A[i]|B[i]));
    end
end
endmodule
```

NEG module:

```
module NEG (A, negresult);

input [31:0] A;
output [31:0] negresult;

reg [31:0] negresult;

integer i;

always @(A)
begin
    for (i = 0; i < 32; i = i + 1)
    begin
        negresult[i] = ~A[i];
    end
    //two's compliment part
    negresult = negresult + 1;
end
endmodule
```

Shift Left module:

```
module SHL(

input [31:0] A, B,
output reg [31:0] shlresult

);

always @(A or B)
begin
    shlresult = A << B;
end
endmodule
```

Shift Right module:

```
module SHR(  
input [31:0] A, B,  
output reg [31:0] shrresult  
);  
always @(A or B)  
begin  
shrresult = A >> B;  
end  
endmodule
```

Shift Right Arithmetic Module:

```
module SHRA(  
input signed [31:0] A, B,  
output reg [31:0] shraresult  
);  
always @(A or B)  
begin  
shraresult = A >>> B;  
end  
endmodule
```

AND module:

```
//AND module  
module AND_mod (A, B, andresult);  
input [31:0] A, B;  
output [31:0] andresult;  
  
reg [31:0] andresult;  
  
integer i;  
always @(A or B)  
begin  
for (i = 0; i < 32; i = i + 1)  
begin  
andresult[i] <= A[i] & B[i];  
end  
end  
endmodule
```

OR module:

```
//OR module
module OR_mod (A, B, orresult);
    input [31:0] A, B;
    output [31:0] orresult;

    reg [31:0] orresult;
    integer i;

    always @(A or B)
    begin
        for (i = 0; i < 32; i = i + 1)
        begin
            orresult[i] = A[i] | B[i];
        end
    end
endmodule
```

Rotate Left module:

```
module ROL(
    input[31:0] A, //value being rotated
    input[31:0] B, //amount of bits A is being rotated
    output reg [31:0] rolresult
);
    always @ (A or B)
    begin
        rolresult = ( A << B ) | ( A >> (32-B));
    end
endmodule
```

Rotate Right module:

```
module ROR(
    input[31:0] A, //value being rotated
    input[31:0] B, //amount of bits A is being rotated
    output reg [31:0] rorresult
);
    always @ (A or B)
    begin
        rorresult = ( A >> B ) | ( A << (32-B));
    end
endmodule
```

Multiplication module:

```

module MUL(
    input signed [31:0] A, B,
    output [63:0] mulresult
);
    reg[2:0] cc[(32/2)-1: 0]; //carry collection
    reg[31:0] pp[(32/2)-1: 0]; //partial product
    reg [63:0] spp[(32/2)-1: 0]; //signed partial product
    reg [63: 0] product; //final

    wire[32:0] inv_a;
    assign inv_a = {~A[31], ~A} + 1; //2's complement of A to be used for booth's algo

    integer j,i;

    always @ (A or B or inv_a) begin
        cc[0] = {B[1], B[0], 1'b0}; //concat two first bits, last bit is carry

        for (j=1;j<(32/2);j=j+1)
            begin
                cc[j] = {B[2*j+1], B[2*j], B[2*j-1]};
            end

        //Calculate the partial product for each of the bits depending on the bit-pair encoding found above
        for (j=0; j<(32/2); j=j+1)
            begin
                case(cc[j])

                    //+1M
                    3'b001, 3'b010 : pp[j] = {A[32-1], A};
                    //+2M
                    3'b011 : pp[j] = {A, 1'b0};
                    //-2M
                    3'b100 : pp[j] = {inv_a[32-1:0], 1'b0};
                    //-1M
                    3'b101, 3'b110 : pp[j] = {inv_a[32-1], inv_a};
                    //0
                    default : pp[j] = 0;
                endcase
                //Convert them to signed partial products
                spp[j] = $signed(pp[j]) << (j*2);
            end
        product = spp[0];

        //sum up the products to obtain the final result
        for (j=1; j<(32/2); j = j+1)
            begin
                product = product +spp[j];
            end
        end
        assign mulresult = product;
    endmodule

```

NOT module:

```

//NOT module
module NOT_mod (A, notresult);
input [31:0] A;
output [31:0] notresult;
reg [31:0] notresult;
integer i;
always @(A)
begin
    for (i = 0; i < 32; i = i + 1)
        begin
            notresult[i] = ~A[i];
        end
    end
endmodule

```

Subtraction Module:

```

module SUB(
input [31:0] A, B,
output reg [31:0] subresult
);
reg [31:0] negB;
reg [32:0] LocalCarry;
integer i;
always@(A or B)
begin
    negB = ~B + 1;
    LocalCarry = 32'b0;
    for(i = 0; i < 32; i = i + 1)
        begin
            subresult[i] = A[i]^negB[i]^LocalCarry[i];
            LocalCarry[i+1] = (A[i]&negB[i])|(LocalCarry[i]&(A[i]|negB[i]));
        end
    end
endmodule


```


Divide Module

```
module DIV(  
input [31:0] A, B,  
output reg [63:0] Divresult  
);  
  
reg [31:0] Q, Rem, Div;  
reg [31:0] temp_Rem; //define file specific variables  
integer y;  
  
always @(*) begin  
    Q = 0;  
    Rem = 0;  
    Div = B;  
    temp_Rem = A; //initilize all variables starting with A  
  
    for (y = 31; y >= 0; y = y - 1) begin  
        //loop through all bits from input register  
  
        //start the non-restorative formula shifting remainder left by one bit  
        Rem = Rem << 1;  
  
        Rem[0] = temp_Rem[31]; //prepaire the next bit to be to used from divisor  
  
        temp_Rem = temp_Rem << 1; //set temp remainder after shift, non restorative so no need to reset  
  
        //loop condition to determine if remainder will be positive or negative to determine if 0 or 1 will be added to Q  
        if (Rem >= Div) begin  
            //calculate new remainder after subtracting the div  
            Rem = Rem - Div;  
            Q = (Q << 1) | 1; // Set the last bit to 1  
        end else begin  
            Q = Q << 1; // Set the last bit to 0  
        end  
    end  
  
    // Adding together quotient with remainder for final  
    Divresult[31:0] = Q;  
    Divresult[63:32] = Rem;  
end  
endmodule
```

Test Bench Used in to create waveforms and test code via manual inputs for 3.1 -3.13:

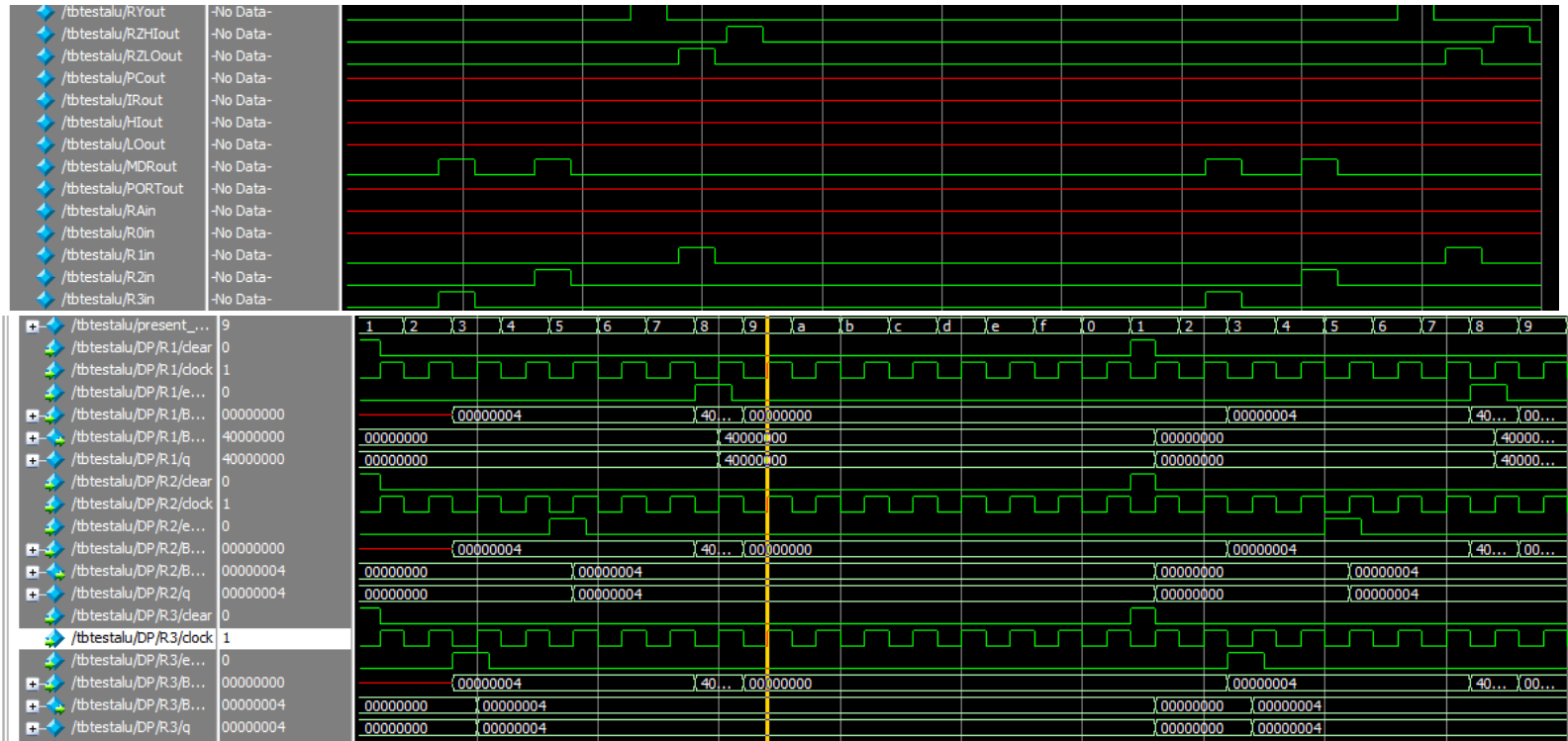Test Bench and Simulation for 3.10 RoR R1, R2, R3:




Modified testbench control sequence:

```
initial begin clock = 0; present_state = 4'd0; end
always #10 clock = ~clock;
always @ (negedge clock) present_state = present_state + 1;

always @(present_state) begin
  case(present_state)
    init: begin
      clear <= 1; Read <= 1;
      Mdatain <= 8'h00; ops <= 5'b0110;
      RZLOout <= 0; MDRout <= 0; MDRin <= 0; R1out <= 0; R1in <= 0; R2in <= 0; R2out <= 0; R3in <= 0; R3out <= 0; RZin <= 0; RYin <= 0; RYout <= 0;
      #10 clear <= 0;
    end
    T0: begin
      Mdatain <= 32'b100; MDRin <= 1;
      //Mdatain <= 32'hffffffd; MDRin <= 1; //for testing SHR AND SHRA
      #15 Mdatain <= 8'h0000; MDRin <= 0;
    end
    T1: begin
      MDRout <= 1; R3in <= 1;
      #15 MDRout <= 0; R3in <= 0;
    end
    T2: begin
      MDRin <= 1; Mdatain <= 32'b100;
      #15 MDRin <= 0; Mdatain <= 8'h0000;
    end
    T3: begin
      MDRout <= 1; R2in <= 1;
      #15 MDRout <= 0; R2in <= 0;
    end
    T4: begin
      R3out <= 1; RYin <= 1;
      #15 R3out <= 0; RYin <= 0;
    end
    T5: begin
      RZin <= 1; R2out <= 1; RYout <= 1;
      #15 RZin <= 0; R2out <= 0; RYout <= 0;
    end
    T6: begin
      RZLOout <= 1; R1in <= 1;
      #15 R1in <= 0; RZLOout <= 0;
    end
    T7: begin
      RZHIout <= 1; HIin <= 1;
      #15 HIin <= 0; RZHIout <= 0;
    end
  endcase
end
endmodule
```

 Test Bench and Simulation for 3.11 Rol R1, R2, R3:



```

module tbtestalu();
reg clock, clear;

reg RAout, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out,
RYout, RZHIout, RZLOout, PCout, IRout, HIout, LOout, MDROUT, PORTout;

reg RAIN, ROin, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in, R14in, R15in,
RYin, RZin, PCin, IRin, HIin, LOin, MDROUT, PORTin, Read;

reg [31:0] Mdatain;

reg [4:0] ops;

reg [3:0] present_state;

DataPath DP(
    clock, clear,
    Mdatain, ops,

    RAout, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out,
    RYout, RZHIout, RZLOout, PCout, IRout, HIout, LOout, MDROUT, PORTout,

    RAIN, ROin, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in, R14in, R15in,
    RYin, RZin, PCin, IRin, HIin, LOin, MDROUT, PORTin, Read
);

```

```


parameter init = 4'd1, T0 = 4'd2, T1 = 4'd3, T2 = 4'd4, T3 = 4'd5, T4 = 4'd6, T5 = 4'd7, T6 = 4'd8, T7 = 4'd9;

initial begin clock = 0; present_state = 4'd0; end
always #10 clock = ~clock;
always @ (negedge clock) present_state = present_state + 1;

always @(present_state) begin
    case(present_state)
        init: begin
            clear <= 1; Read <= 1;
            Mdatain <= 8'h00; ops <= 5'b00111;
            RZLOout <= 0; MDRout <= 0; RIout <= 0; MDRin <= 0; Rlin <= 0; R2in <= 0; R2out <= 0; R3in <= 0; R3out <= 0; RZin <= 0; RYin <= 0; RYout <= 0;
            RZHIout <= 0; HIin <= 0;
            #10 clear <= 0;
        end
        T0: begin
            //Mdatain <= 32'b1001; MDRin <= 1;
            Mdatain <= 32'hfffffff; MDRin <= 1; //for testing SHR AND SHRA
            #15 Mdatain <= 8'h0000; MDRin <= 0;
        end
        T1: begin
            MDRout <= 1; R3in <= 1;
            #15 MDRout <= 0; R3in <= 0;
        end
        T2: begin
            MDRin <= 1; Mdatain <= 32'b100;
            #15 MDRin <= 0; Mdatain <= 8'h0000;
        end
        T3: begin
            MDRout <= 1; R2in <= 1;
            #15 MDRout <= 0; R2in <= 0;
        end
        T4: begin
            R3out <= 1; RYin <= 1;
            #15 R3out <= 0; RYin <= 0;
        end
        T5: begin
            RZin <= 1; R2out <= 1; RYout <= 1;
            #15 RZin <= 0; R2out <= 0; RYout <= 0;
        end
        T6: begin
            RZLOout <= 1; Rlin <= 1;
            #15 Rlin <= 0; RZLOout <= 0;
        end
        T7: begin
            RZHIout <= 1; HIin <= 1;
            #15 HIin <= 0; RZHIout <= 0;
        end
    endcase
end
endmodule

```

 Test Bench and Simulation for 3.12 neg R6, R7:



Changed Control Sequence:

```


parameter init = 4'd1, T0 = 4'd2, T1 = 4'd3, T2 = 4'd4, T3 = 4'd5, T4 = 4'd6, T5 = 4'd7, T6 = 4'd8, T7 = 4'd9;

initial begin clock = 0; present_state = 4'd0; end
always #10 clock = ~clock;
always @ (negedge clock) present_state = present_state + 1;

always @(present_state) begin
    case(present_state)
        init: begin
            clear <= 1; Read <= 1;
            Mdatain <= 8'h00; ops <= 5'b00100;
            RZLOout <= 0; MDRout <= 0; MDRin <= 0; R6out <= 0; R6in <= 0; R7in <= 0; R7out <= 0; R3in <= 0; R3out <= 0; RZin <= 0; RYin <= 0; RYout <= 0;
            #10 clear <= 0;
        end
        T0: begin
            Mdatain <= 32'b100; MDRin <= 1;
            //Mdatain <= 32'hfffffffd; MDRin <= 1; //for testing SHR AND SHRA
            #15 Mdatain <= 8'h0000; MDRin <= 0;
        end
        T1: begin
            MDRout <= 1; R7in <= 1;
            #15 MDRout <= 0; R7in <= 0;
        end
        T2: begin
            MDRin <= 1; Mdatain <= 32'b100;
            #15 MDRin <= 0; Mdatain <= 8'h0000;
        end
        T3: begin
            MDRout <= 1; R1in <= 1;
            #15 MDRout <= 0; R1in <= 0;
        end
        T4: begin
            R7out <= 1; RYin <= 1;
            #15 R7out <= 0; RYin <= 0;
        end
        T5: begin
            RZin <= 1; R2out <= 1; RYout <= 1;
            #15 RZin <= 0; R2out <= 0; RYout <= 0;
        end
        T6: begin
            RZLOout <= 1; R6in <= 1;
            #15 R6in <= 0; RZLOout <= 0;
        end
        T7: begin
            RZHIout <= 1; HIin <= 1;
            #15 HIin <= 0; RZHIout <= 0;
        end
    endcase
end
endmodule

```

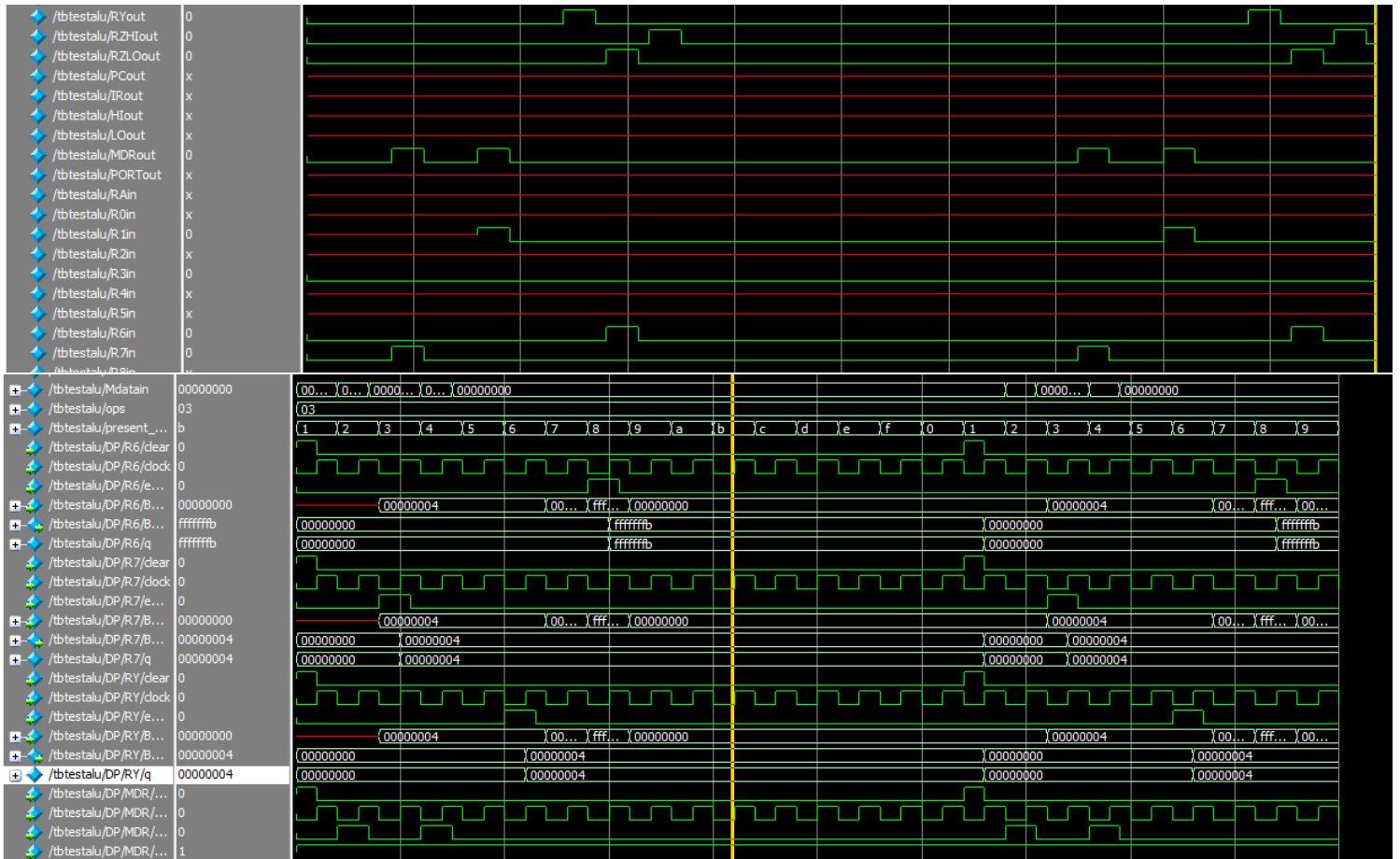Test Bench and Simulation for 3.13 not R6, R7



Modified Testbench control sequence:

```
parameter init = 4'd1, T0 = 4'd2, T1 = 4'd3, T2 = 4'd4, T3 = 4'd5, T4 = 4'd6, T5 = 4'd7, T6 = 4'd8, T7 = 4'd9;

initial begin clock = 0; present_state = 4'd0; end
always #10 clock = ~clock;
always @ (negedge clock) present_state = present_state + 1;

always @(present_state) begin
  case(present_state)
    init: begin
      clear <= 1; Read <= 1;
      Mdatain <= 8'h00; ops <= 5'b00011;
      RZLOout <= 0; MDROUT <= 0; MDRin <= 0; R6out <= 0; R6in <= 0; R7in <= 0; R7out <= 0; R3in <= 0; R3out <= 0; RZin <= 0; RYin <= 0; RYout <= 0;
      RZHIout <= 0; HIin <= 0;
      #10 clear <= 0;
    end
    T0: begin
      Mdatain <= 32'b100; MDRin <= 1;
      //Mdatain <= 32'hffffffd; MDRin <= 1; //for testing SHR AND SHRA
      #15 Mdatain <= 8'h0000; MDRin <= 0;
    end
    T1: begin
      MDROUT <= 1; R7in <= 1;
      #15 MDROUT <= 0; R7in <= 0;
    end
    T2: begin
      MDRin <= 1; Mdatain <= 32'b100;
      #15 MDRin <= 0; Mdatain <= 8'h0000;
    end
    T3: begin
      MDROUT <= 1; R1in <= 1;
      #15 MDROUT <= 0; R1in <= 0;
    end
    T4: begin
      R7out <= 1; RYin <= 1;
      #15 R7out <= 0; RYin <= 0;
    end
    T5: begin
      RZin <= 1; R2out <= 1; RYout <= 1;
      #15 RZin <= 0; R2out <= 0; RYout <= 0;
    end
    T6: begin
      RZLOout <= 1; R6in <= 1;
      #15 R6in <= 0; RZLOout <= 0;
    end
    T7: begin
      RZHIout <= 1; HIin <= 1;
      #15 HIin <= 0; RZHIout <= 0;
    end
  endcase
end
endmodule
```